University of Rajshahi
Department of Computer Science and Engineering
B.Sc. Engineering Part-I Even Semester Examination 2021
Course: CSE1212-Introduction to Digital Electronics Lab

[Solve the following Tick marked questions.]

1. Design and implement 2-bit adder ~~subtractor~~ adder using gates.
2. Design a logic circuit that has four inputs, A, B, C, and D, and whose outputwill be HIGH when only any two inputs are High, and the output is LOW otherwise.
3. Design and implement the parity bit generator and checker circuit.
4. Design and implement the code conversion circuit from binary to gray code and viceversa.
5. Design and implement an enabled JK flip flop.

CamScanner